

# Computer-Aided Design for VLSI Design

Homework1 ( Student ID: 41147046S | Name: 楊子萱 )

1. Provide a simple explanation of your code.

Hw1 的設計，可供後續直接使用

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity My_ckt_1 is
6  Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
7        B : in STD_LOGIC_VECTOR (7 downto 0);
8        S : in STD_LOGIC_VECTOR (1 downto 0);
9        Y : out STD_LOGIC_VECTOR (15 downto 0));
10 end My_ckt_1;
11
12 architecture Behavioral of My_ckt_1 is
13 begin
14     process (A, B, S)
15     begin
16         case S is
17             when "00" => -- Mode 1: Bitwise OR
18                 Y(7 downto 0) <= STD_LOGIC_VECTOR(UNSIGNED(A) OR UNSIGNED(B));
19                 Y(15 downto 8) <= (others => '0');
20
21             when "01" => -- Mode 2: Multiplication
22                 Y <= STD_LOGIC_VECTOR(RESIZE(UNSIGNED(A) * UNSIGNED(B), 16));
23
24             when "10" => -- Mode 3: Addition
25                 Y <= STD_LOGIC_VECTOR(RESIZE(UNSIGNED(A) + UNSIGNED(B), 16));
26
27             when "11" => -- Mode 4: Modulus
28                 if UNSIGNED(B) /= 0 then
29                     Y(7 downto 0) <= STD_LOGIC_VECTOR(RESIZE(UNSIGNED(A) MOD UNSIGNED(B), 8));
30                     Y(15 downto 8) <= (others => '0');
31                 else
32                     Y <= (others => '0'); -- ??K???H?s???~
33                 end if;
34
35             when others =>
36                 Y <= (others => '0');
37         end case;
38     end process;
39 end Behavioral;
```

D 型正反器的設計

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity D_FF is
5  Port (
6      clk : in STD_LOGIC;
7      D   : in STD_LOGIC_VECTOR;
8      Q   : out STD_LOGIC_VECTOR
9  );
10 end D_FF;
11
12 architecture Behavioral of D_FF is
13 begin
14     process(clk)
15     begin
16         if rising_edge(clk) then
17             Q <= D;
18         end if;
19     end process;
20 end Behavioral;
21

```

定義模組名稱為 My\_ckt\_2，輸入為 clk, A, B, S，輸出為 Y。

```

4  entity My_ckt_2 is
5  Port (
6      clk : in STD_LOGIC;
7      A   : in STD_LOGIC_VECTOR(7 downto 0);
8      B   : in STD_LOGIC_VECTOR(7 downto 0);
9      S   : in STD_LOGIC_VECTOR(1 downto 0);
10     Y   : out STD_LOGIC_VECTOR(15 downto 0)
11 );
12 end My_ckt_2;

```

訴編譯器我們稍後會在此模組中用到 D\_FF 和 My\_ckt\_1，這兩個是子模組。

```

17  component D_FF
18  Port (
19      clk : in STD_LOGIC;
20      D   : in STD_LOGIC_VECTOR;
21      Q   : out STD_LOGIC_VECTOR
22  );
23  end component;
24
25  component My_ckt_1
26  Port (
27      A : in STD_LOGIC_VECTOR(7 downto 0);
28      B : in STD_LOGIC_VECTOR(7 downto 0);
29      S : in STD_LOGIC_VECTOR(1 downto 0);
30      Y : out STD_LOGIC_VECTOR(15 downto 0)
31  );
32  end component;

```

定義內部的中介訊號，用來連接 flip-flop 與 My\_ckt\_1，並暫存資料。

```

34  -- 中介線路
35  signal A_reg, B_reg : STD_LOGIC_VECTOR(7 downto 0);
36  signal S_reg       : STD_LOGIC_VECTOR(1 downto 0);
37  signal Y_temp      : STD_LOGIC_VECTOR(15 downto 0);
38  signal Y_reg       : STD_LOGIC_VECTOR(15 downto 0);

```

每個輸入都先經過 D flip-flop 暫存，以實現同步輸入。

```

42  DFF_A : D_FF
43      port map(clk => clk, D => A, Q => A_reg);
44
45  -- 註冊輸入 B
46  DFF_B : D_FF
47      port map(clk => clk, D => B, Q => B_reg);
48
49  -- 註冊輸入 s
50  DFF_S : D_FF
51      port map(clk => clk, D => S, Q => S_reg);
52
53  -- 註冊輸出 Y
54  DFF_Y : D_FF
55      port map(clk => clk, D => Y_temp, Q => Y_reg);

```

呼叫之前寫好的 My\_ckt\_1 模組，進行加法、乘法等運算，輸出結果給

Y\_temp。

```

58      U1 : My_ckt_1
59      port map(
60          A => A_reg,
61          B => B_reg,
62          S => S_reg,
63          Y => Y_temp
64      );

```

把 D flip-flop 的輸出送到頂層輸出 Y


```

67      Y <= Y_reg;

```

## 2. Waveform diagram here (Simulation Results)

波形圖含在.zip 中

 

## 3. Reflections and discussions

在此設計中，考量到乘法運算時兩個 8 位元輸入可能產生 16 位元結果，因此需使用 UNSIGNED 型別搭配 RESIZE，以避免位元溢位問題。針對 MOD 運算，需避免除以 0 的未定義行為，因此透過 if 條件判斷來確保輸出穩定。另一方面，本電路採用 D flip-flop 並以時脈控制輸出，確保輸出僅在上升沿更新，具有時序同步的特性。從模擬結果可觀察到輸出 Y 會隨著 clk 的 rising edge 對應更新輸出值，使整體電路在時序控制與資料鎖存方面更具可靠性與一致性。